

→* Chapter → 1 *

→* Circuit Analysis *

* Circuit → Web of element which forms a closed loop.

* Circuit element → Resistor, Inductor and capacitor

→ Resistor → $V = IR$ (Ohm's Law)
Resistance ← property of resistor

→ Inductor →

symbol →
"~~~~~"

$$\Psi = N\phi$$

$$\phi \propto I$$

$$N\phi \propto I$$

$$N\phi = LI$$

$$L = \frac{N\phi}{I}$$

→ Capacitor →

Symbol -


"—||—"

$$Q \propto V$$

$$[Q = CV]$$

charge → capacitance

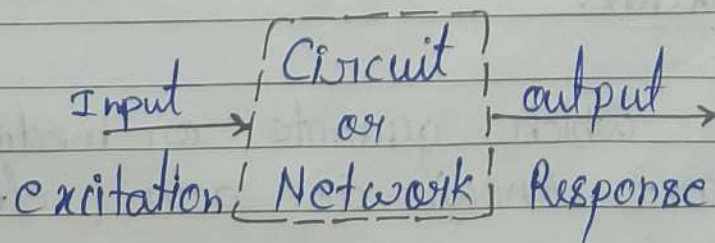⊕ Network → Web of elements which may or may not form closed loop are called Network.



Basic Quantities: →

a) Current (I) or (i) →

$$I = \frac{dq}{dt} \rightarrow \text{unit: amperes (A)}$$

↓

Rate of flow of charge

b) Voltage → Energy per unit charge between two points, in volts.

$$V = \frac{Kq}{r} \quad \text{or} \quad V = \frac{dW}{dq}$$

c) Power → Energy per unit time

$$P = \frac{dW}{dt} \quad P = \frac{dW}{dt} \times \frac{dq}{dq} \quad P = VI \quad \text{or}$$

$$P = \frac{V^2}{R}$$

unit:- watts (W)

d) Energy → $W = \int P \cdot dt$

Types of elements →

a) Active elements:-

The element which generate or modify the signals are known as active elements.

ex → Diode, Transistor, Amplifier, Battery etc.

b) Passive elements →

Those elements which are unable to change (generate) or modify the signal are called passive elements.

ex → Inductor, Transistor, Capacitor etc.

⑧ Linear and Non-Linear elements →

a) Linear → The elements that characteristics are straight line and passing through origin is known as linear elements.

ex → Resistor, Inductor, Capacitor etc.

a) Bilateral

b) Non-Linear → Those elements that offers different in in both direction of current flow.

ex → Diode, HCR etc.

b) Non-Linear → Those element that characteristics not a straight line is known as non-linear elements.


ex → Diode, HCR etc.

HCR → High Rupturing Capacity fuse

⑧ Unilateral and Bilateral elements →

b) Bilateral → The elements that offers same in both the direction of current flow.

SOURCE

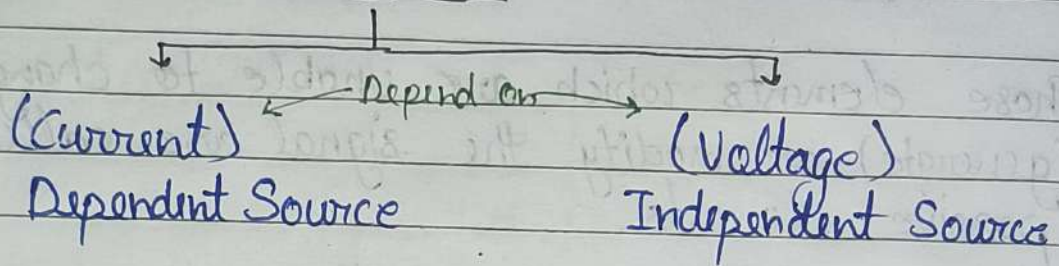

→ voltage dependent voltage source $K_v V_x$


→ current dependent voltage source $K_y I_y$

→ current dependent voltage source $K_y I_y$


→ voltage dependent current source $K_x V_x$

→ Current Source

Ideal
 $R_{SH} = \infty$

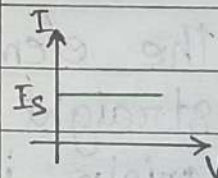


practical
 R_{SH}

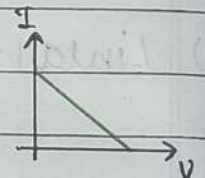


→ Voltage Source

Ideal
 $R_s = 0$

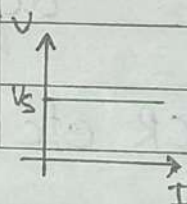


Practical
 R_s

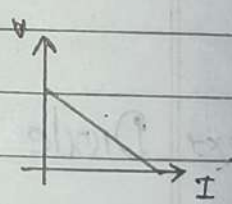


⑧ Current Source →



$$R_{SH} = \frac{V_{oc}}{I_{sc}}$$

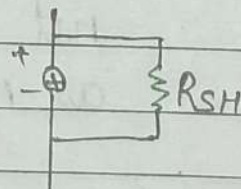

⑧ Voltage Source →

$$R_s = \frac{V_{oc}}{I_{sc}}$$

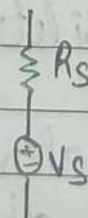

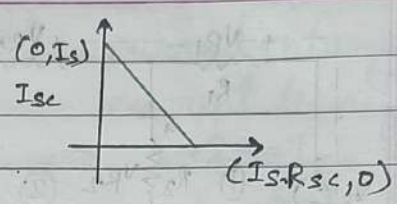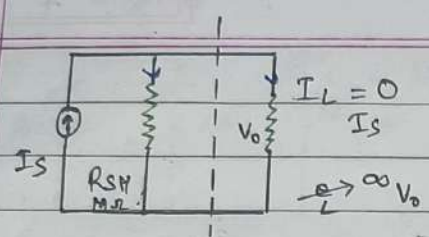

$$I_L = I_S = I_{sc}$$

$$R_{sc} = \frac{\text{O.C. Voltage}}{\text{S.C. current}}$$


Kirchhoff's Current Law (KCL) →

for any lumped circuit the algebraic sum of current entering or leaving a node is equal to zero at any instant of time.


It depends on conservation of charge.

$$Q_1 + Q_2 = Q_3 + Q_4$$

$$I_1 + I_2 = I_3 + I_4$$

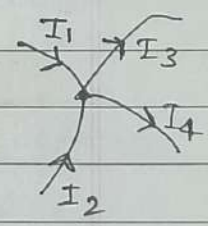

Example ①

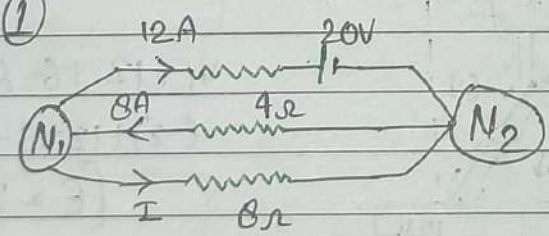


Solve:

$$8 = 12 + I$$

$$I = 12 - 8 = 8 - 12 = -4 \text{ A}$$

Example ②

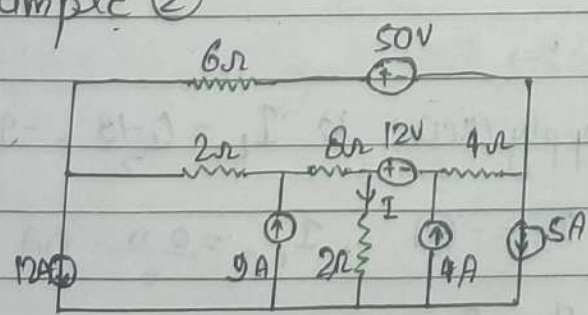


total incoming current = total outgoing current

$$9 + 4 = 12 + I + 5$$


$$I = 13 - 17$$

$$I = -4 \text{ A}$$

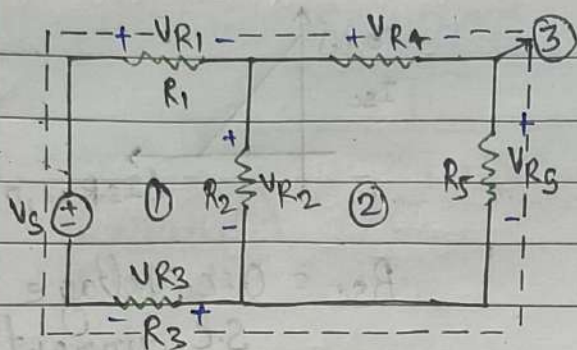

→ The sum of voltage drop across in each element in any loop is equal to zero. it is based on conservation of law.

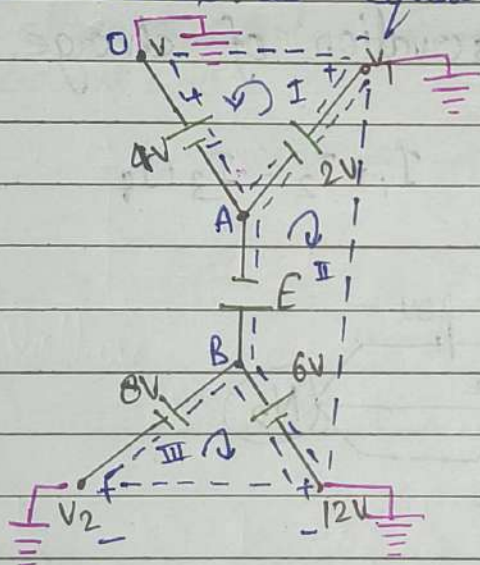The algebraic sum of node voltage for any closed nodes is equal to zero.



$$2 - V_1 - 0 - 4 = 0$$

$$[V_1 = -2V]$$

$$V_1 + 12 + 6 - E + 2 = 0$$


$$-(-2) + 12 + 6 - E + 2 = 0$$

$$[E = 22V]$$

$$8 - 6 - 12 + V_2 = 0$$

$$V_2 = 10$$

Ques find the value of I :-

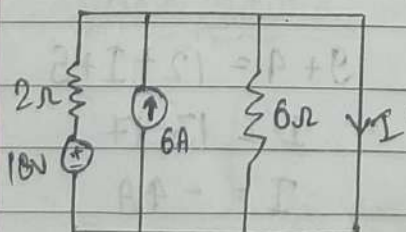


apply (KCL) → $I_L = \frac{0-10}{2} = -5A$

$$I_s = -6A, I_{6A} = \frac{0-0}{6} = 0A$$

$$I_R = I$$

$$-9 - 6 + 0 + I = 0 \Rightarrow -15 + I = 0$$

$$[I = 15A]$$

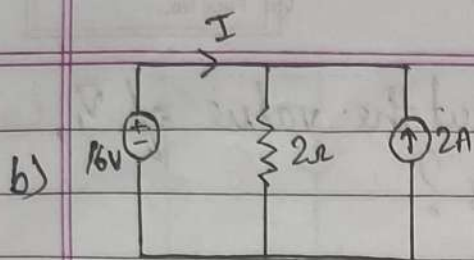


$$I_{2\Omega} = \frac{16}{2} = 8A$$

current entering =
current leaving

$$I + 2A = I_{2\Omega} = 8A$$

$$I = 8 - 2 = 6A$$

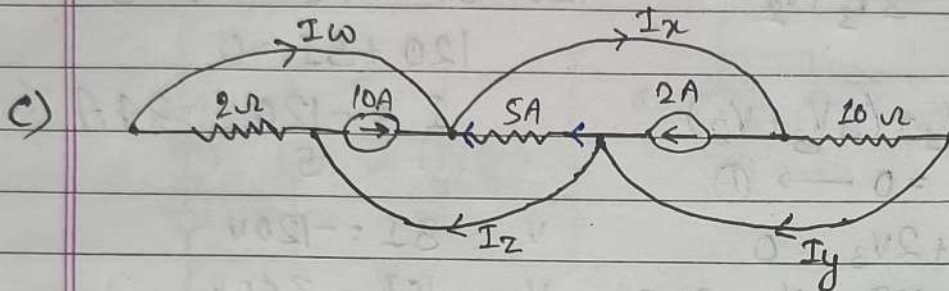


$$10 + I_w + I_{5A} = I_x \quad | \quad I_z = I_w + 10$$

$$\boxed{I_w = 0; I_x = 10A} \quad | \quad 2 + I_y - I_{5A} - I_z = 0$$

$$I_z = 10;$$
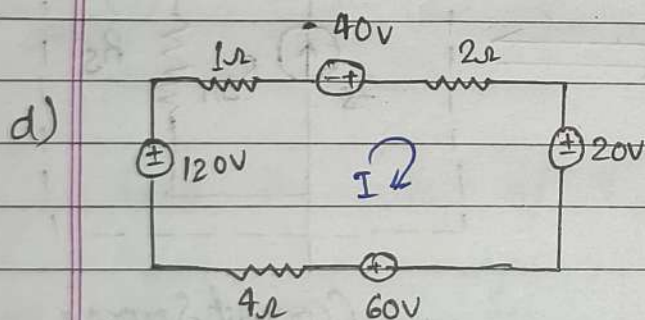
$$I_z = I_y + 2 \Rightarrow I_y = 10 - 2 = 8A$$



$$-I(1) + 40 - I(2) - 20 - 60 - I(4) + 120 = 0$$

$$(-1-2-4)I + (40+20-60+120) = 0$$


$$-7I + 80 = 0$$

$$7I = 80$$

$$I = \frac{80}{7} \approx 11.43A$$

28/09/26

e)

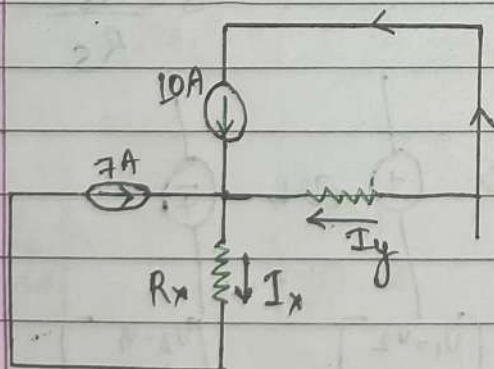

find the value of I_x and I_y .


solve

$$\boxed{I_x = 7A}$$

$$I_y = -10A \Rightarrow 7 + 10 + I_y = I_x$$

$$7 + 10 + I_y = 7$$

$$\boxed{I_y = -10A}$$

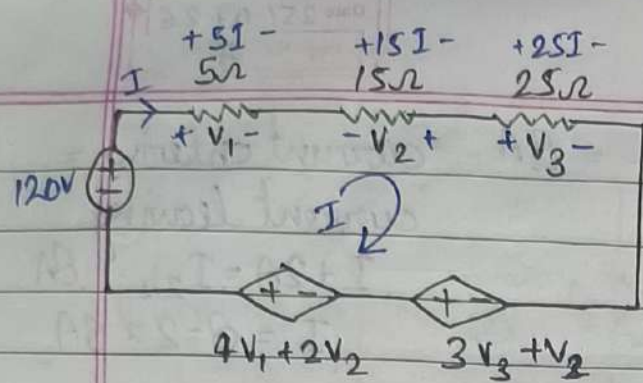

find out the value of V_1 , V_2 , V_3 ?

$$120 + 15I - 60I + 50I = 0$$

$$120 + 5I = 0$$

$$I = \frac{-120}{5} = -24A$$

Using
KVL

$$120 - V_1 + V_2 - V_3 + (3V_3 + V_2) + (4V_1 + 2V_2) = 0 \rightarrow (1)$$

$$\Rightarrow 120 + 3V_1 + 4V_2 + 2V_3 = 0$$




$$V_1 = 5I, V_2 = -15I, V_3 = 25I$$

$$V_1 = 5I = -120V$$

$$V_2 = -15I = 360V$$

$$V_3 = 25I = -600V$$

Source Transformation $\rightarrow$


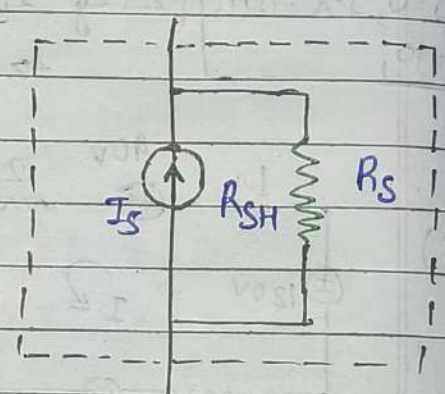
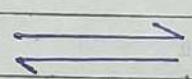
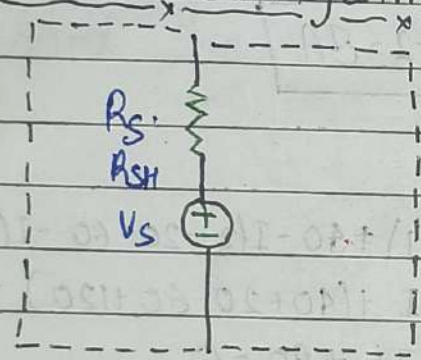




Voltage Source

$$V_S = I_S \cdot R_{SH}$$




Current Source


$$I_S = \frac{V_S}{R_S}$$

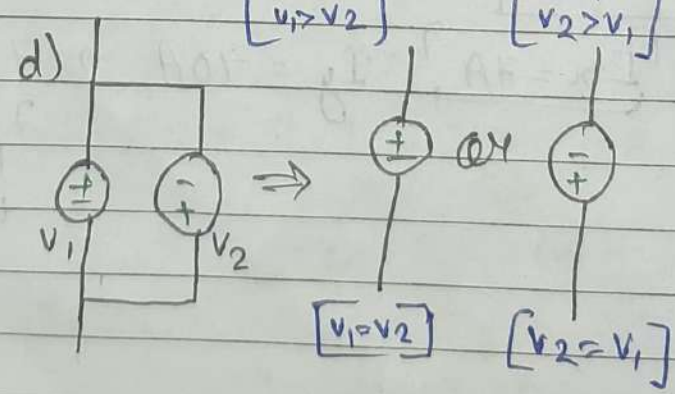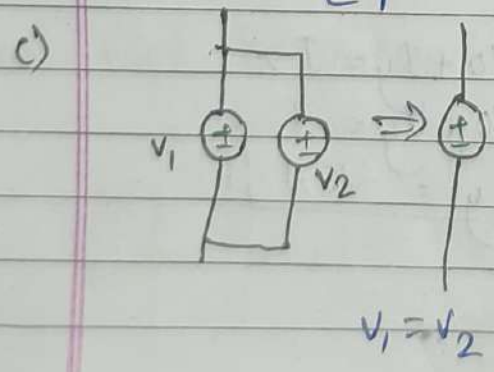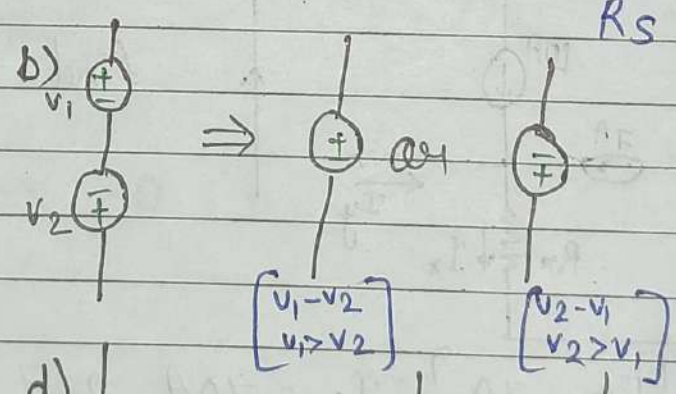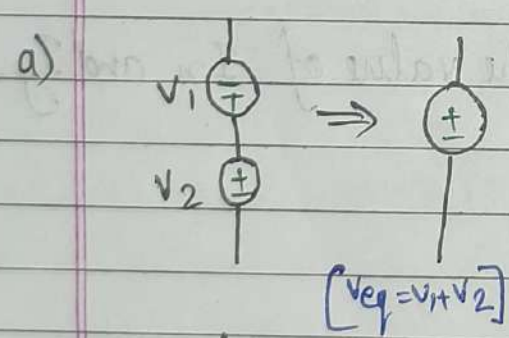

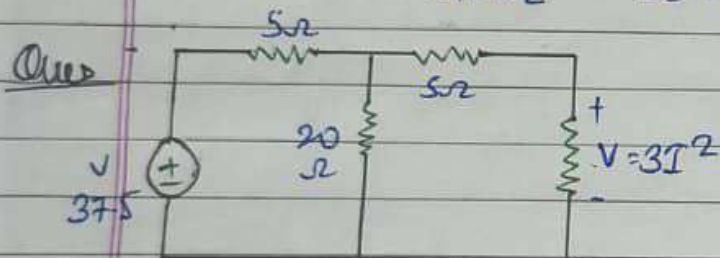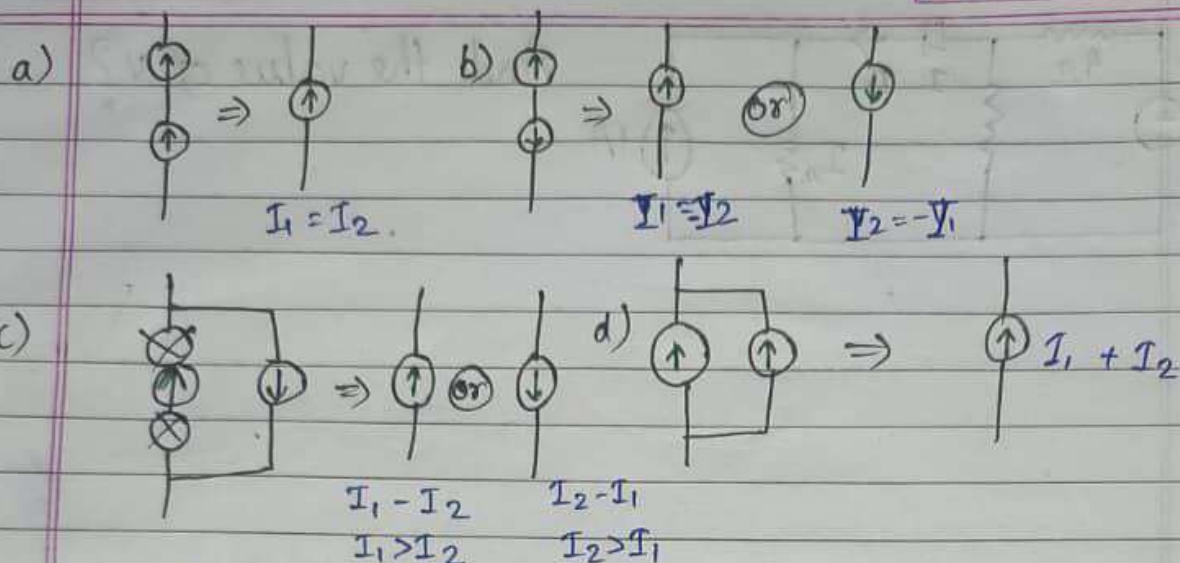

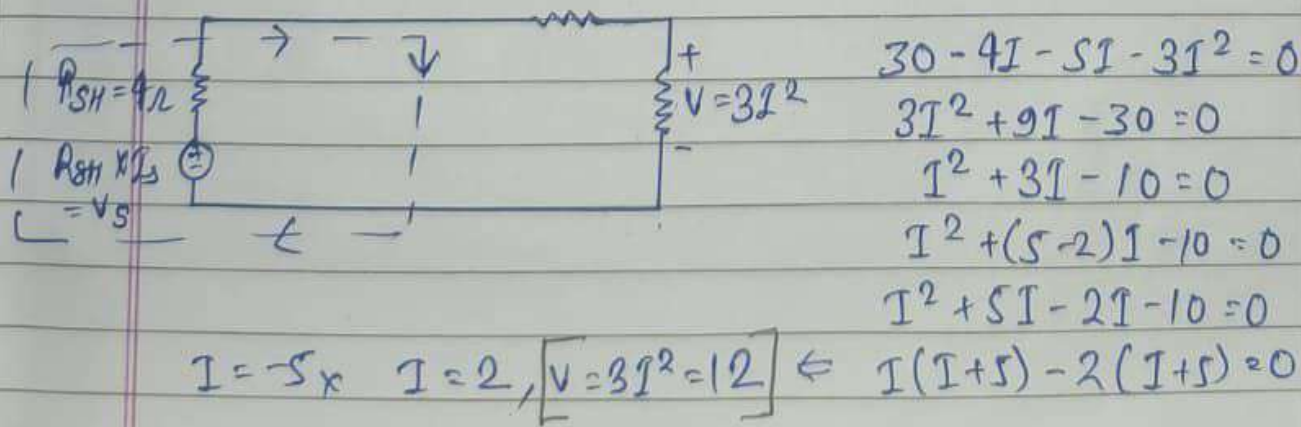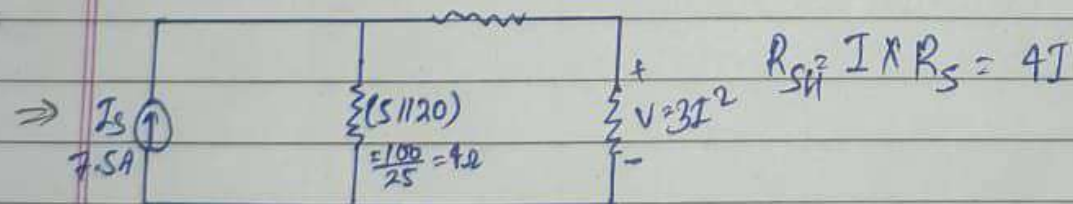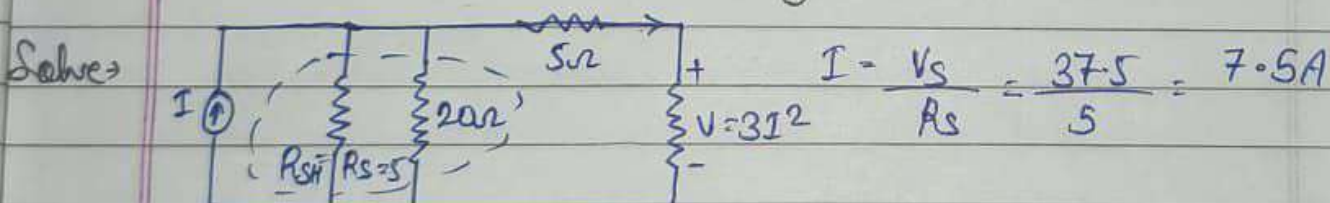find the value of V using source transformation?



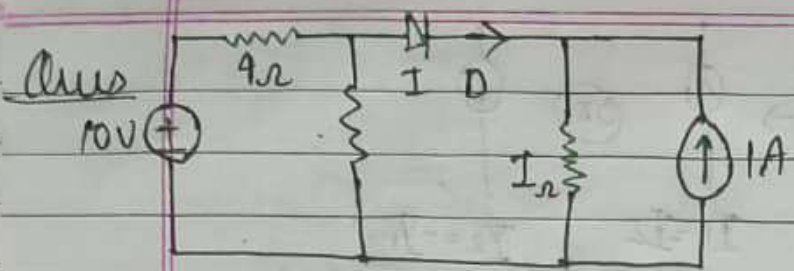

find the value of V ?

find the value of V using nodal analysis

$$10 - 4I_1 - I_2 = 0 \quad \text{--- (1)}$$

$$I_2 = 1 \quad \text{--- (2)}$$

$$I_1 = 2.5 \text{ A}$$

$$V = 10 - 4(2.5) - 1(1)$$

$$V = 10 - 10 - 1$$

$$V = -1 \text{ V}$$

$$V = -1 \text{ V}$$

$$V = -1 \text{ V}$$

$$V = -1 \text{ V}$$